
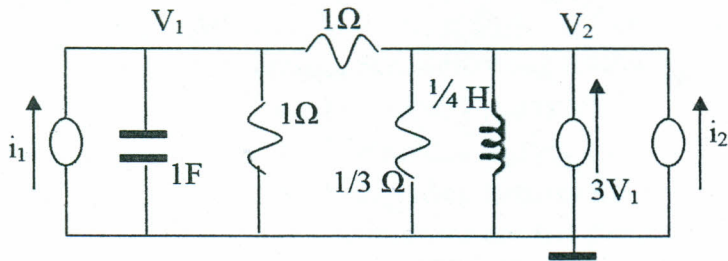


Attempt the following.

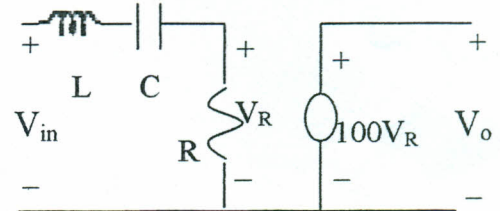- For circuit (A) find the time response $v_2(t)$ given $i_1(t) = t U(t)$, $i_2(t) = e^{-2t} U(t)$. and the initial conditions are specified as ; $V_0 = 1/4$ volts and $I_0 = 0$. (15pts)
- For circuit (B) find the voltage transfer function V_o/V_{in} . Choose suitable values for R, L, and C that yield a circuit suitable to select inputs within 1 – 10 kHz frequency band . (10pts)



(A)



(B)

- Determine the function corresponding to the Bode magnitude plot shown in Fig (1). (10pts)
- Write the matrix state equation for the circuit shown in Fig.(2). (10pts)

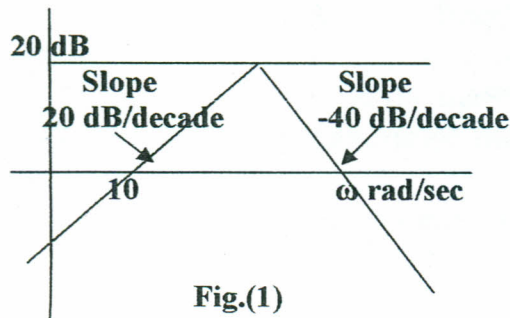


Fig.(1)


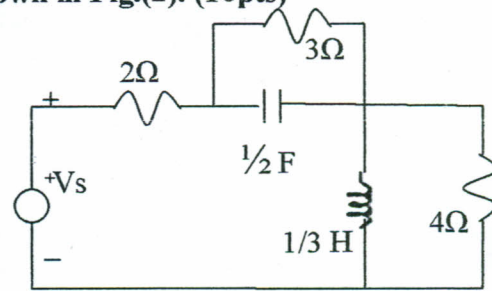


Fig.(2)

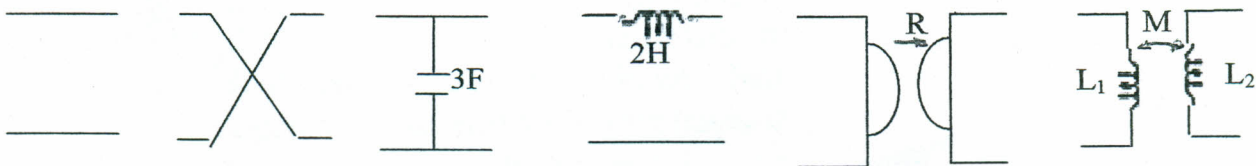- Find the transmission parameters (ABCD) for each of the two ports in the figure below (10pts)



- For Fig.(3) find the scattering parameters for the two port shown when double terminated by one ohm resistances. (15pts)

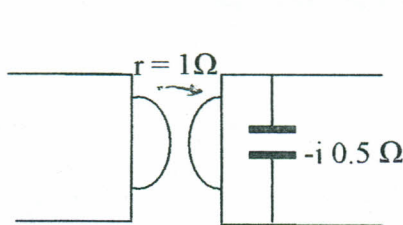


Fig.(3)

- In Fig. (4) the two transistors are identical and each has a CE y parameters $Y_{ine} = 1 S$, $Y_{re} = 0$, $Y_{fe} = 10 S$, and $Y_{oe} = 0.1 S$. Write the IAM of the circuit, and find V_o/V_{in} (15pts)

What will be V_o/V_{in} if transistors are ideal (10pts)?

- Find the input impedance Z_{in} for the circuit shown in Fig.(5). Assuming ideal Op Amp. (15pts)

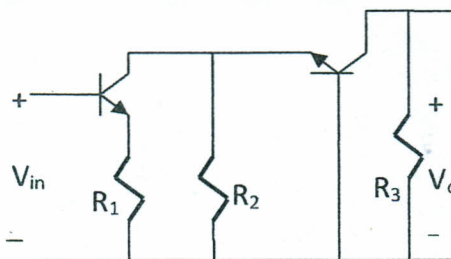


Fig.(4)

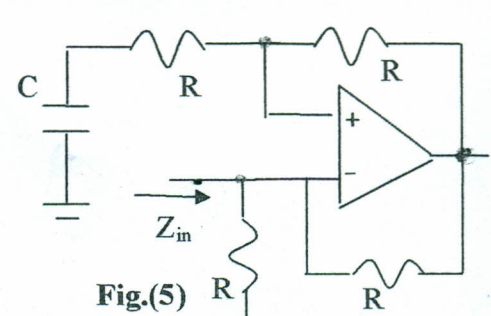


Fig.(5)

Full Mark 100 pts

Good Luck.