

(بسم الله الرحمن الرحيم *** لا إله إلا الله محمد رسول الله)



جامعة المنوفية كلية الهندسة بشبين الكوم قسم الهندسة الكهربائية

الدراسات العليا: دكتوراه مادة: تحليل التوافقيات في محركات الجر ELE719

الفصل الدراسي الثاني 2019-2020 م التاريخ: الخميس 13/8/2020 النهاية: 100 درجة

Answer the following questions [25 Marks for each]

Question1: a)- What do you know about: 1- Non-sinusoidal wave . 2-Odd function . 3-Even function . 4-Fourier series .

b)- A full-wave rectified voltage has the following Fourier series expansion;
 $e = 314/\pi [1 + 2/3 \cos 2\omega t - 2/15 \cos 4\omega t + 2/35 \cos 6\omega t + \dots]$, $\omega = 314 \text{ rad/sec}$.
This voltage is applied across an inductive coil has 100Ω resistance & 0.1 H inductance.
Find the coil current as Fourier series, the average power loss and the over-all power factor .

Question2: (a)-What are the principle sources of harmonics in electrical networks?

(b)- The transients in electric circuits may be a source of harmonics .

Discus the dc transients for R-L & R-C circuits .

c)-The switch S in the circuit of Fig.1 is closed for long time and open until the coil current finished. The circuit parameters are; $E=24\text{V}$, $R_1=R_2 =1\Omega$, $L=1 \text{ H}$ & $C= 1\text{F}$. Find the coil current at on & off cases .

Question3: (a)- What do you know about the Fourier analyzer?

(b)- A three- phase generator has an EMF of 11 KV/phase , 50Hz with 15% third harmonic and 10% fifth harmonic. Calculate: 1 –the r.m.s value of line voltage for four-line, star-connection . 2—the r.m.s value of line voltage for delta-connection . 3-the circulating current in delta- connection if ($R = 0.5\Omega$ & $L = 1\text{H}$) / phase .

Question4: (a)- Electronic control of electric motors may be a big source of harmonics in electric networks, discuss the half-wave rectifier with R-L load.

b)- Figure 2, shows An inverter circuit has the following parameters; $E=48\text{V}$, $R=0.01\Omega$, $L=0.2 \text{ H}$. Draw the waves of the gat currents, the output voltage across the load and the instantaneous current throw it.

c)- A chopper-driven for DC series motor is shown in Fig.3. The motor voltage and the expected steady-state armature current are given, also. The data pertaining to the motor and chopper are: $R=8\text{m}\Omega$, $L=0.025 \text{ mH}$, $K_a= 8$, $\lambda=1 \text{ sec.}$, $\alpha =0.6$ and $V_t =24 \text{ V}$. Obtain the motor torque-speed and η -speed. The motor magnetization characteristic is given as :

$I_{av} , \text{ m A}$	5000	4600	4200	3800	3200	2250
Flux/pole, m Wb	2.25	3.2	3.8	4.2	4.6	5.0

الحمد لله رب العالمين

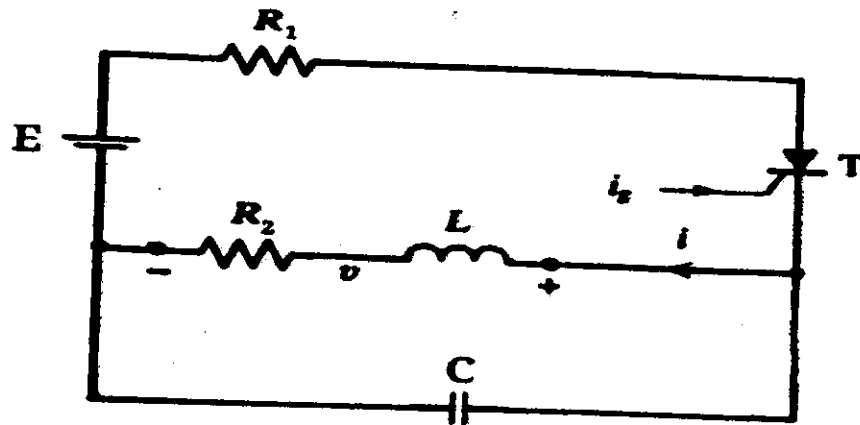


Fig.(1)

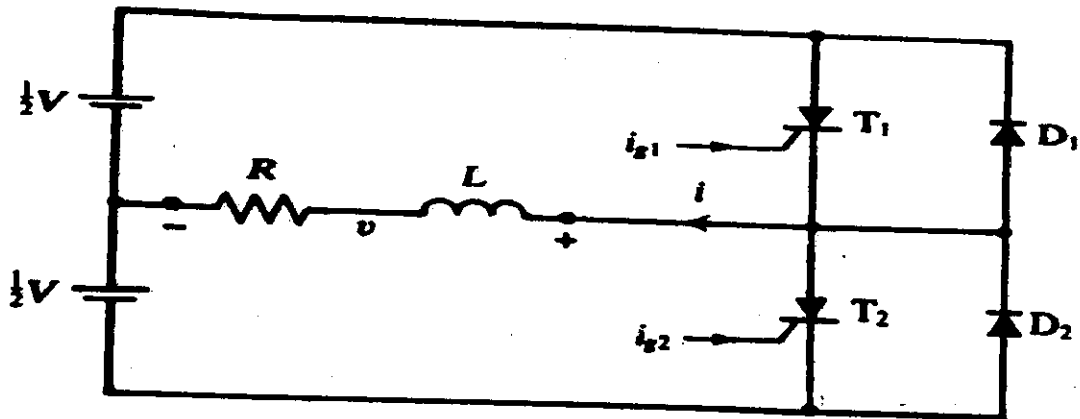


Fig.(2)

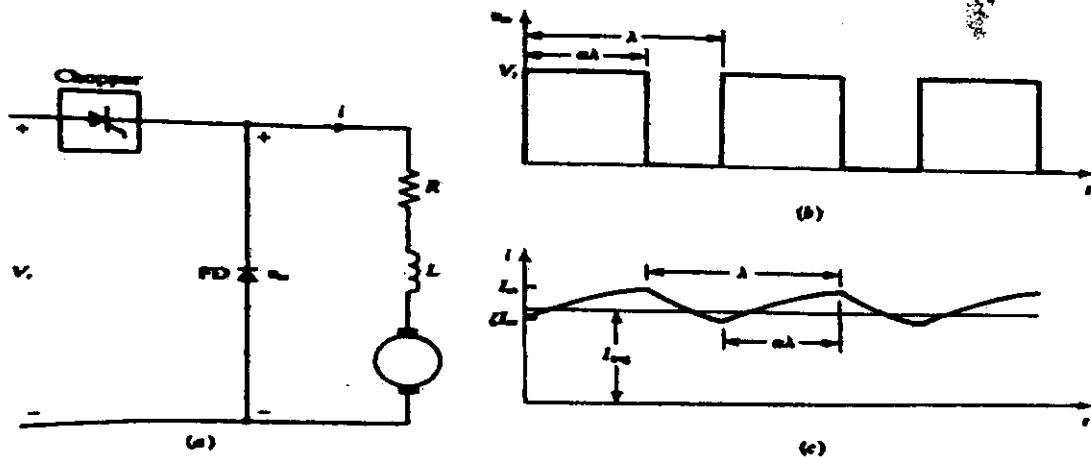


Fig.(3)

Good Luck

الحمد لله رب العالمين