

Mansoura University Faculty of Engineering Electronics and Communications Engineering Department
--

Digital Circuits 1 - Term Exam	Exam Time: 3 hours
1st year Communications - 2nd Term	Total Marks: 70 Marks
Exam Date: June 04, 2014	

Important Instructions:

1 This exam contains:

20 Questions (Fill the blanks with pre-selected words) --> Write ONLY your answers in the answer booklet (10 Marks; 0.5 Mark each)

15 MCQs (4 choices each) --> Mark your answer selection in the MCQ answer sheet in the middle of the answer booklet Q1-Q15 (15 Marks; 1 Mark each)

20 Questions (True/False) --> Mark your answer selection in the MCQ answer sheet in the middle of the answer booklet Q16-Q35 (10 Marks; 0.5 Mark each)

Mark ① for TRUE answer and mark ② for FLASE answer.

2 Questions (Regular technical questions) --> Write your answers in the booklet (35 Marks)

My best wishes to YOU!

Dr. Sameh Rehan

Note: This exam has questions on both sides of the questions' sheets.

Q13 This is the truth table for a(n) _____.

- ① NAND
- ② NOR
- ③ AND
- ④ OR

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Q14 This is the truth table for a(n) _____.

- ① NAND
- ② NOR
- ③ AND
- ④ OR

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Q15 This is the truth table for a(n) _____.

- ① NAND
- ② NOR
- ③ AND
- ④ OR

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Answer the following 20 TRUE/FALSE questions in the dedicated MCQ answer sheet

Q16-Q35 in the answer booklet:

(10 Marks; 0.5 Mark each)

Q16 6 binary digits are required to count to decimal 100.

Q17 In binary addition, $10 + 11 = 21$.

Q18 In binary multiplication, $11 \times 11 = 1001$.

Q19 In binary division, $1000 \div 0100 = 100$.

Q20 In binary subtraction, $101-11 = 10$.

Q21 The decimal number system consists of the digits 0-10.

Q22 The largest numerical value that is possible with a 4-bit binary number is 16.

Q23 The largest single digit in the octal numbering system is 7.

Q24 A circle, or bubble, on a distinctive-shape logic symbol indicates a logic inversion.

Q25 The OR gate performs as switches wired in series.

Q26 The output of a 2-input XNOR gate is 1 when the inputs are equal, or identical.

Q27 The output of an AND gate is HIGH only when all inputs are HIGH.

Q28 When the inputs to a 3-input OR gate are 001, the output is 1.

Q29 When the inputs to a 3-input NAND gate are 001, the output is 1.

Q30 When the inputs to a 3-input NOR gate are 001, the output is 1.

Q31 The XOR gate can be used to add two bits.

Q32 DeMorgan's theorem states that:

$$\overline{XY} = X+Y$$

Q33 The commutative law of Boolean addition states that $A + B = A . B$.

Q34 The Karnaugh maps provide 'cookbook' approaches to simplifying Boolean expressions.

Q35 When grouping cells in a Karnaugh map, the cells must be combined in groups of 2's.


Fill the blanks (by selecting from the listed set of words) in the answer booklet for the following questions:

(NOT, OR, AND, NAND, NOR, XOR, XNOR, rise time, fall time, amplitude, transition time, period, pulse width, zero, infinite, positive-going edge, negative-going edge, Multiplexer, Demultiplexer, Encoder, Decoder, Comparator, Register, LOW, HIGH) (10 Marks; 0.5 Mark each)


- S1. On a digital waveform, the transition time from a HIGH level to a LOW level is called _____.
 S2. On a digital waveform, the interval between pulses is called _____.
 S3. For an ideal digital pulse, transition times are _____.
 S4. For a negative-logic pulse, the leading edge is the _____.

In the shown nonideal pulse:

 - S5. Item (1) represents _____.
 S6. Item (2) represents _____.
 S7. Item (3) represents _____.
 S8. Item (4) represents _____.



 - S9. The device in Fig. (A) is a(n) _____ function.
 S10. The device in Fig. (B) is a(n) _____ function.
 S11. The device in Fig. (C) is a(n) _____ function.




- S12. The _____ circuit creates an output that indicates whether or not the input values are equal.
 S13. The _____ circuit converts information into a specific coded form.
 S14. The _____ circuit converts data from a serial to a parallel form.
 S15. The _____ circuit is made up of flip-flops.
 S16. In the 2-input _____ gate, a Low input gives a High output.
 S17. In the 2-input _____ gate, a High input gives a Low output.
 S18. In the 2-input _____ gate, a Low input gives a Low output.
 S19. In the 2-input _____ gate, a High input gives a High output.
 S20. In the NOT digital circuit, a _____ input gives a High output.

Answer the following regular questions in the answer booklet:

(2 questions - total of 35 Marks)

- R1. For a two binary number multiplier (each consists of 2 bits): (15 Marks)
 a- write the truth table of the multiplier. (4 Marks)
 b- what is the optimized Boolean expressions for the first two least-significant-bits (LSBs) of the multiplier outputs. (6 Marks)
 c- implement the logic circuits for the optimized expressions using only NAND gates. (5 Marks)

 - R2. For the 7-segment decoding logic, a BCD number is used as the input and the 7 outputs are used to activate the corresponding segments of the display. The arrangement of segments is as shown here: (total of 20 marks)



- a- write down the truth table (use X to represent don't care output) for all 7 segments. (7 Marks)
 b- develop the optimized Boolean logic expression of the "e" output segment. (8 marks)
 c- develop the optimized logic circuit for segment "e". (5 marks)

Note: complements of inputs are available.