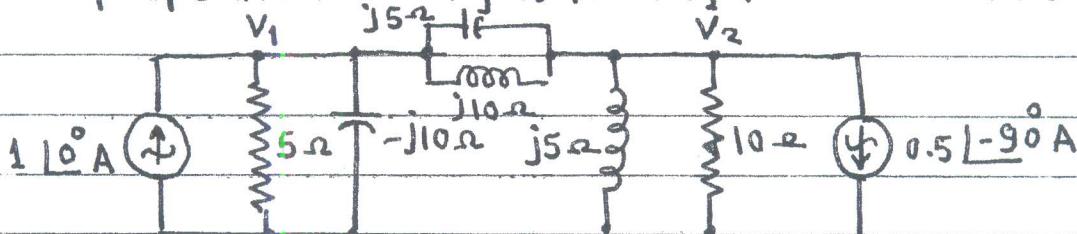


PART II Alternating CurrentAnswer The following Questions:-

1. a. State the Superposition Theory

1. b. Use Superposition Theory to find V_1 for the circuit shown2. a. Derive The instantaneous power entering a circuit $p(t)$ 2. b. The voltage across a load is $v(t) = 6 \cos(\omega t - 10^\circ)$ V and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ)$ A Find:


(a) the complex and apparent powers.

(b) the real and reactive powers, and (c) the power factor and the load impedance.

3. a. Derive the relation between the input impedance Z_{in} and load impedance Z_L and turns ratio a in ideal transformer

$$Z_{in} = \frac{Z_L}{a^2} \text{ for finite } Z_L$$

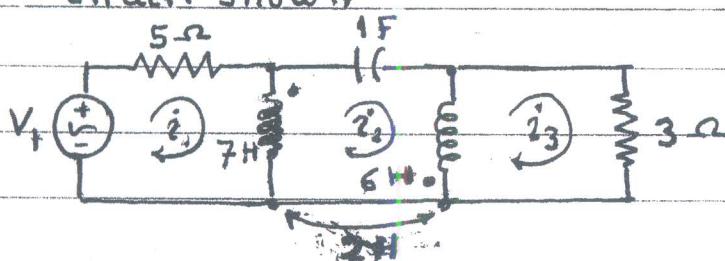3. b. Write a complete set of phasor mesh equations for the circuit shown



with Best Wishes!!